


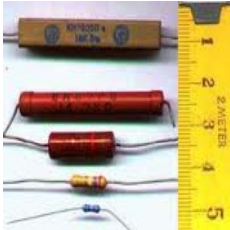




EEE 2015 ELECTRICS

L03 AC Circuit Analysis & Power Calculations

L02 Alternating Voltage and Current

Behaviors of Basic Circuit Components under AC

Resistor (R)	Coil (L) (Inductor)	Capacitor (C) (Condenser)
Resistor 100 Ω  $R = 100 \Omega$ $X = 0 \Omega$ $Z = 100 \Omega \angle 0^\circ$	Inductor 100 mH 159.15 Hz  $R = 0 \Omega$ $X = 100 \Omega$ $Z = 100 \Omega \angle 90^\circ$	Capacitor 10 μF 159.15 Hz  $R = 0 \Omega$ $X = 100 \Omega$ $Z = 100 \Omega \angle -90^\circ$
		

Dr. Levent ÇETİN

L02 Alternating Voltage and Current

AC circuit –RL in series

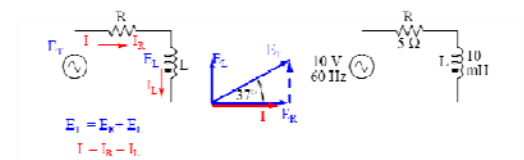


Figure 3.10: Series resistor inductor circuit. Current lags applied voltage by 0° to 90°.

Inductive reactance of the coil

$$X_L = 0 + 3.7699j\Omega$$

The total effect is called as **impedance**.

$$Z = R + X_L = 5 + 3.7699j\Omega = 6.262\angle 37.016^\circ\Omega$$

$$Z = \frac{V}{I}$$

$$I = \frac{10\angle 0^\circ}{6.262\angle 37.016^\circ} = 1.597\angle -37.016^\circ\text{A}$$

Dr. Levent ÇETİN

L02 Alternating Voltage and Current

AC circuit –RL in series

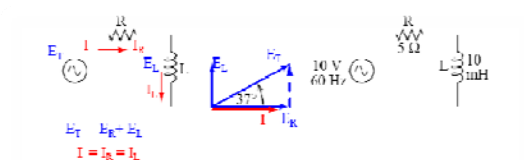


Figure 3.10: Series resistor inductor circuit. Current lags applied voltage by 0° to 90°.



Figure 3.11: Current lags voltage in a series L-R circuit.

$$E = IZ$$

$$E = IZ$$

$$E_R = I_R Z_R$$

$$E_L = I_L Z_L$$

$$E_R = (1.597\text{ A} \angle -37.016^\circ)(5\Omega \angle 0^\circ)$$

$$E_L = (1.597\text{ A} \angle -37.016^\circ)(3.7699\Omega \angle 90^\circ)$$

$$E_R = 7.9847\text{ V} \angle -37.016^\circ$$

$$E_L = 6.0203\text{ V} \angle 52.984^\circ$$

Notice that the phase angle of E_L is exactly 90° more than the phase angle of the current.

$$E_{\text{total}} = E_R + E_L$$

$$E_{\text{total}} = (7.9847\text{ V} \angle -37.016^\circ) + (6.0203\text{ V} \angle 52.984^\circ)$$

$$E_{\text{total}} = 10\text{ V} \angle 0^\circ$$

Dr. Levent ÇETİN

L02 Alternating Voltage and Current

AC circuit –RL in parallel

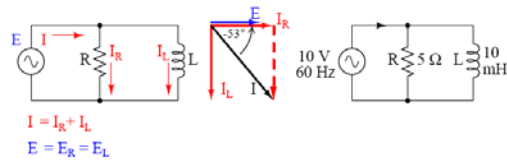


Figure 3.14: Parallel R-L circuit.

	R	L	Total	
E	10 + j0 10 ∠ 0°	10 + j0 10 ∠ 0°	10 + j0 10 ∠ 0°	Volts
I				Amps
Z	5 + j0 5 ∠ 0°	0 + j3.7699 3.7699 ∠ 90°		Ohms

Rule of parallel circuits:
 $E_{total} = E_R = E_L$

Dr. Levent ÇETİN

L02 Alternating Voltage and Current

AC circuit –RL in parallel

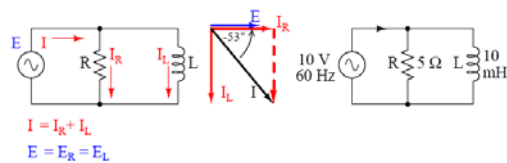


Figure 3.14: Parallel R-L circuit.

	R	L	Total	
E	10 + j0 10 ∠ 0°	10 + j0 10 ∠ 0°	10 + j0 10 ∠ 0°	Volts
I	2 + j0 2 ∠ 0°	0 - j2.6526 2.6526 ∠ -90°		Amps
Z	5 + j0 5 ∠ 0°	0 + j3.7699 3.7699 ∠ 90°		Ohms

Ohm's Law
 $I = \frac{E}{Z}$

Ohm's Law
 $I = \frac{E}{Z}$

Dr. Levent ÇETİN

L02 Alternating Voltage and Current

AC circuit –RL in parallel

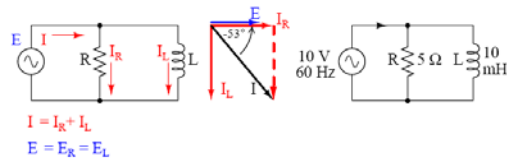


Figure 3.14: Parallel R-L circuit.

	R	L	Total	
E	10 + j0 10 \angle 0°	10 + j0 10 \angle 0°	10 + j0 10 \angle 0°	Volts
I	2 + j0 2 \angle 0°	0 - j2.6526 2.6526 \angle -90°	2 - j2.6526 3.3221 \angle -52.984°	Amps
Z	5 + j0 5 \angle 0°	0 + j3.7699 3.7699 \angle 90°		Ohms

Rule of parallel circuits:
 $I_{\text{total}} = I_R + I_L$

Dr. Levent ÇETİN

L02 Alternating Voltage and Current

AC circuit –RL in parallel

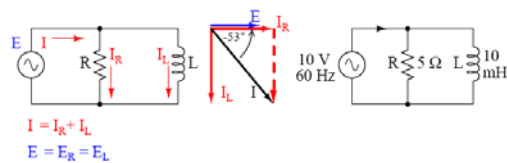


Figure 3.14: Parallel R-L circuit.

	R	L	Total	
E	10 + j0 10 \angle 0°	10 + j0 10 \angle 0°	10 + j0 10 \angle 0°	Volts
I	2 + j0 2 \angle 0°	0 - j2.6526 2.6526 \angle -90°	2 - j2.6526 3.322 \angle -52.984°	Amps
Z	5 + j0 5 \angle 0°	0 + j3.7699 3.7699 \angle 90°	1.8122 + j2.4035 3.0102 \angle 52.984°	Ohms

Ohm's Law
 $Z = \frac{E}{I}$


or

Rule of parallel circuits:
 $Z_{\text{total}} = \frac{1}{\frac{1}{Z_R} + \frac{1}{Z_L}}$

Dr. Levent ÇETİN

L02 Alternating Voltage and Current

AC circuit –RC in series

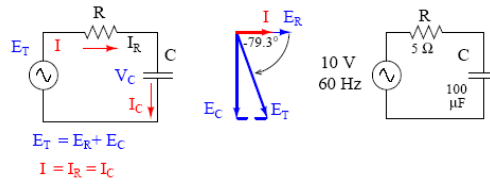

$$X_C = 0 - 26.5258j\Omega$$

$$R = 5 + 0j\Omega$$

$$Z = R + X_C = 5 - 26.5258j\Omega = 26.993\angle -79.325$$

$$I = \frac{E}{Z}$$

$$I = \frac{10\text{ V} \angle 0^\circ}{26.933\Omega \angle -79.325^\circ}$$

$$I = 370.5\text{ mA} \angle 79.325^\circ$$


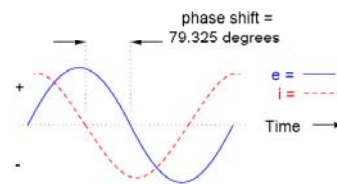


Figure 4.11: Voltage lags current (current leads voltage) in a series R-C circuit.

Dr. Levent ÇETİN

L02 Alternating Voltage and Current

AC circuit –RC in series

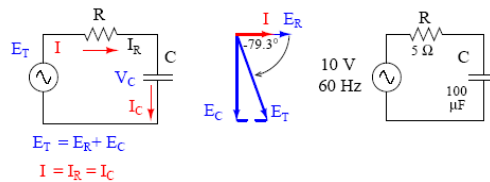

	R	C	Total	
E			10 + j0 10 ∠ 0°	Volts
I			68.623m + j364.06m 370.5m ∠ 79.325°	Amps
Z	5 + j0 5 ∠ 0°	0 - j26.5258 26.5258 ∠ -90°	5 - j26.5258 26.993 ∠ -79.325°	Ohms


	R	C	Total	
E			10 + j0 10 ∠ 0°	Volts
I	68.623m + j364.06m 370.5m ∠ 79.325°	68.623m + j364.06m 370.5m ∠ 79.325°	68.623m + j364.06m 370.5m ∠ 79.325°	Amps
Z	5 + j0 5 ∠ 0°	0 - j26.5258 26.5258 ∠ -90°	5 - j26.5258 26.993 ∠ -79.325°	Ohms

Rule of series
circuits:
 $I_{\text{total}} = I_R = I_C$

Dr. Levent ÇETİN

L02 Alternating Voltage and Current

AC circuit –RC in series

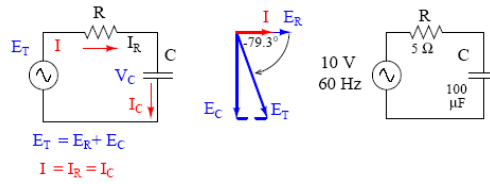

	R	C	Total	
E	343.11m + j1.8203 1.8523 \angle 79.325°	9.6569 - j1.8203 9.8269 \angle -10.675°	10 + j0 10 \angle 0°	Volts
I	68.623m + j364.06m 370.5m \angle 79.325°	68.623m + j364.06m 370.5m \angle 79.325°	68.623m + j364.06m 370.5m \angle 79.325°	Amps
Z	5 + j0 5 \angle 0°	0 - j26.5258 26.5258 \angle -90°	5 - j26.5258 26.993 \angle -79.325°	Ohms

Ohm's Law $E = IZ$ Ohm's Law $E = IZ$


As it can be considered easily, the phase shift is 79.325 degrees in this circuit whereas in the circuit that has only one capacitor it was 90 degrees.

The current and the voltage on the resistor is on the same phase as it is mentioned. However, the current on a capacitor leads voltage by 90 degrees.

Dr. Levent ÇETİN

L02 Alternating Voltage and Current

AC circuit –RC in parallel

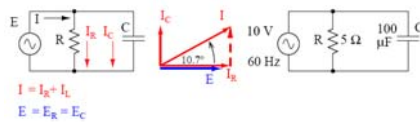

	R	C	Total	
E			10 + j0 10 \angle 0°	Volts
I				Amps
Z	5 + j0 5 \angle 0°	0 - j26.5258 26.5258 \angle -90°		Ohms

	R	C	Total	
E	10 + j0 10 \angle 0°	10 + j0 10 \angle 0°	10 + j0 10 \angle 0°	Volts
I				Amps
Z	5 + j0 5 \angle 0°	0 - j26.5258 26.5258 \angle -90°		Ohms


Rule of parallel circuits:

$$E_{\text{total}} = E_R = E_C$$

Dr. Levent ÇETİN

L02 Alternating Voltage and Current

AC circuit –RC in parallel

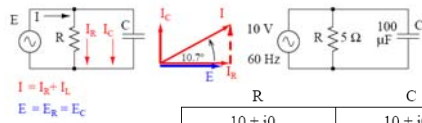

$$I = I_R + I_C$$

$$E = E_R = E_C$$

Figure

	R	C	Total	
E	$10 + j0$ $10 \angle 0^\circ$	$10 + j0$ $10 \angle 0^\circ$	$10 + j0$ $10 \angle 0^\circ$	Volts
I	$2 + j0$ $2 \angle 0^\circ$	$0 + j376.99\text{m}$ $376.99\text{m} \angle 90^\circ$		Amps
Z	$5 + j0$ $5 \angle 0^\circ$	$0 - j26.5258$ $26.5258 \angle -90^\circ$		Ohms

Ohm's Law

$$I = \frac{E}{Z}$$

Ohm's Law

$$I = \frac{E}{Z}$$

	R	C	Total	
E	$10 + j0$ $10 \angle 0^\circ$	$10 + j0$ $10 \angle 0^\circ$	$10 + j0$ $10 \angle 0^\circ$	Volts
I	$2 + j0$ $2 \angle 0^\circ$	$0 + j376.99\text{m}$ $376.99\text{m} \angle 90^\circ$	$2 + j376.99\text{m}$ $2.0352 \angle 10.675^\circ$	Amps
Z	$5 + j0$ $5 \angle 0^\circ$	$0 - j26.5258$ $26.5258 \angle -90^\circ$		Ohms


Rule of parallel circuits:

$$I_{\text{total}} = I_R + I_C$$

Dr. Levent ÇETİN

L02 Alternating Voltage and Current

AC circuit –RC in parallel

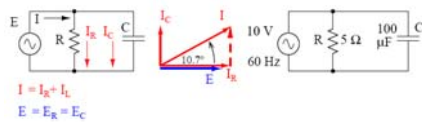

$$I = I_R + I_C$$

$$E = E_R = E_C$$

Figure 4.14: Parallel R-C circuit.

	R	C	Total	
E	$10 + j0$ $10 \angle 0^\circ$	$10 + j0$ $10 \angle 0^\circ$	$10 + j0$ $10 \angle 0^\circ$	Volts
I	$2 + j0$ $2 \angle 0^\circ$	$0 + j376.99\text{m}$ $376.99\text{m} \angle 90^\circ$	$2 + j376.99\text{m}$ $2.0352 \angle 10.675^\circ$	Amps
Z	$5 + j0$ $5 \angle 0^\circ$	$0 - j26.5258$ $26.5258 \angle -90^\circ$	$4.8284 - j910.14\text{m}$ $4.9135 \angle -10.675^\circ$	Ohms

Ohm's Law

$$Z = \frac{E}{I}$$

or

Rule of parallel circuits:

$$Z_{\text{total}} = \frac{1}{\frac{1}{Z_R} + \frac{1}{Z_C}}$$

Dr. Levent ÇETİN

L02 Alternating Voltage and Current

AC circuit –RLC in series

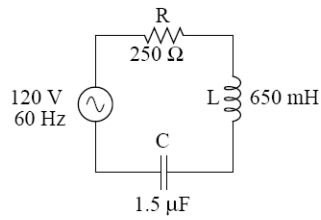


Figure 5.2: Example series R, L, and C circuit.

$$X_L = 2\pi fL$$

$$X_L = (2)(\pi)(60 \text{ Hz})(650 \text{ mH})$$

$$X_L = 245.04 \Omega$$

$$X_C = \frac{1}{2\pi fC}$$

$$X_C = \frac{1}{(2)(\pi)(60 \text{ Hz})(1.5 \mu\text{F})}$$

$$X_C = 1.7684 \text{ k}\Omega$$

$$Z_R = 250 + j0 \Omega \quad \text{or} \quad 250 \Omega \angle 0^\circ$$

$$Z_L = 0 + j245.04 \Omega \quad \text{or} \quad 245.04 \Omega \angle 90^\circ$$

$$Z_C = 0 - j1.7684 \text{ k}\Omega \quad \text{or} \quad 1.7684 \text{ k}\Omega \angle -90^\circ$$

Dr. Levent ÇETİN

L02 Alternating Voltage and Current

AC circuit –RLC in series

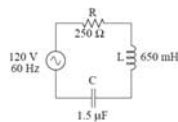


Figure 5.2: Example series R, L, and C circuit.

	R	L	C	Total	
E				120 + j0 120 ∠ 0°	Volts
I					Amps
Z	250 + j0 250 ∠ 0°	0 + j245.04 245.04 ∠ 90°	0 - j1.7684k 1.7684k ∠ -90°		Ohms

	R	L	C	Total	
E				120 + j0 120 ∠ 0°	Volts
I					Amps
Z	250 + j0 250 ∠ 0°	0 + j245.04 245.04 ∠ 90°	0 - j1.7684k 1.7684k ∠ -90°	250 - j1.5233k 1.5437k ∠ -80.680°	Ohms

Rule of series circuits:
 $Z_{\text{total}} = Z_R + Z_L + Z_C$

	R	L	C	Total	
E				120 + j0 120 ∠ 0°	Volts
I				12.589m + j6.708m 77.734m ∠ 80.680°	Amps
Z	250 + j0 250 ∠ 0°	0 + j245.04 245.04 ∠ 90°	0 - j1.7684k 1.7684k ∠ -90°	250 - j1.5233k 1.5437k ∠ -80.680°	Ohms

Ohm's Law
 $I = \frac{E}{Z}$

Dr. Levent ÇETİN

L02 Alternating Voltage and Current

AC circuit –RLC in series

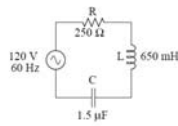


Figure 5.2: Example series R, L, and C circuit.

	R	L	C	Total	
E				$120 + j0$ $120 \angle 0^\circ$	Volts
I	$12.589\text{m} + j6.708\text{m}$ $77.734\text{m} \angle 80.680^\circ$	$12.589\text{m} + j6.708\text{m}$ $77.734\text{m} \angle 80.680^\circ$	$12.589\text{m} + j6.708\text{m}$ $77.734\text{m} \angle 80.680^\circ$	$12.589\text{m} + j6.708\text{m}$ $77.734\text{m} \angle 80.680^\circ$	Amps
Z	$250 + j0$ $250 \angle 0^\circ$	$0 + j245.04$ $245.04 \angle 90^\circ$	$0 - j1.7684\text{k}$ $1.7684\text{k} \angle -90^\circ$	$250 - j1.5233\text{k}$ $1.5437\text{k} \angle -80.680^\circ$	Ohms

Rule of series circuits:
 $I_{\text{total}} = I_R = I_L = I_C$

	R	L	C	Total	
E	$3.1472 + j19.177$ $19.434 \angle 80.680^\circ$	$-18.797 + j3.0848$ $19.048 \angle 170.68^\circ$	$135.65 - j22.262$ $137.46 \angle -9.3199^\circ$	$120 + j0$ $120 \angle 0^\circ$	Volts
I	$12.589\text{m} + j6.708\text{m}$ $77.734\text{m} \angle 80.680^\circ$	$12.589\text{m} + j6.708\text{m}$ $77.734\text{m} \angle 80.680^\circ$	$12.589\text{m} + j6.708\text{m}$ $77.734\text{m} \angle 80.680^\circ$	$12.589\text{m} + j6.708\text{m}$ $77.734\text{m} \angle 80.680^\circ$	Amps
Z	$250 + j0$ $250 \angle 0^\circ$	$0 + j245.04$ $245.04 \angle 90^\circ$	$0 - j1.7684\text{k}$ $1.7684\text{k} \angle -90^\circ$	$250 - j1.5233\text{k}$ $1.5437\text{k} \angle -80.680^\circ$	Ohms

Ohm's Law
 $E = IZ$

$E_R + E_L + E_C$ should equal E_{total}

$3.1472 + j19.177 \text{ V}$	E_R
$-18.797 + j3.0848 \text{ V}$	E_L
$+ 135.65 - j22.262 \text{ V}$	E_C
$120 + j0 \text{ V}$	E_{total}

It should be considered that the amplitude of the voltage on the capacitor is greater than the voltage supplied to the circuit. The influence of the impedance in the whole circuit is smaller than the influence of impedance of any single component. This case causes higher voltages on single components.

Dr. Levent ÇETİN

L02 Alternating Voltage and Current

AC circuit –RLC in paralel

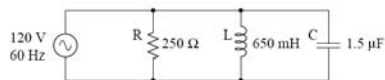


Figure 5.5: Example R, L, and C parallel circuit.

	R	L	C	Total	
E				$120 + j0$ $120 \angle 0^\circ$	Volts
I					Amps
Z	$250 + j0$ $250 \angle 0^\circ$	$0 + j245.04$ $245.04 \angle 90^\circ$	$0 - j1.7684\text{k}$ $1.7684\text{k} \angle -90^\circ$	$245.04 \angle 90^\circ$	Ohms

Rule of parallel circuits:
 $E_{\text{total}} = E_R = E_L = E_C$

	R	L	C	Total	
E	$120 + j0$ $120 \angle 0^\circ$	$120 + j0$ $120 \angle 0^\circ$	$120 + j0$ $120 \angle 0^\circ$	$120 + j0$ $120 \angle 0^\circ$	Volts
I					Amps
Z	$250 + j0$ $250 \angle 0^\circ$	$0 + j245.04$ $245.04 \angle 90^\circ$	$0 - j1.7684\text{k}$ $1.7684\text{k} \angle -90^\circ$		Ohms

Dr. Levent ÇETİN

L02 Alternating Voltage and Current

AC circuit –RLC in paralel



Figure 5.5: Example R, L, and C


	R	L	C	Total	
E	120 + j0 120 ∠ 0°	120 + j0 120 ∠ 0°	120 + j0 120 ∠ 0°	120 + j0 120 ∠ 0°	Volts
I	480m + j0 480m ∠ 0°	0 - j489.71m 489.71m ∠ -90°	0 + j67.858m 67.858m ∠ 90°		Amps
Z	250 + j0 250 ∠ 0°	0 + j245.04 245.04 ∠ 90°	0 - j1.7684k 1.7684k ∠ -90°		Ohms
	↑ Ohm's Law $I = \frac{E}{Z}$	↑ Ohm's Law $I = \frac{E}{Z}$	↑ Ohm's Law $I = \frac{E}{Z}$		

	R	L	C	Total	
E	120 + j0 120 ∠ 0°	120 + j0 120 ∠ 0°	120 + j0 120 ∠ 0°	120 + j0 120 ∠ 0°	Volts
I	480m + j0 480 ∠ 0°	0 - j489.71m 489.71m ∠ -90°	0 + j67.858m 67.858m ∠ 90°	480m - j421.85m 639.03m ∠ -41.311°	Amps
Z	250 + j0 250 ∠ 0°	0 + j245.04 245.04 ∠ 90°	0 - j1.7684k 1.7684k ∠ -90°	141.05 + j123.96 187.79 ∠ 41.311°	Ohms

Dr. Levent ÇETİN

L02 Alternating Voltage and Current

AC circuit –Complex Circuit

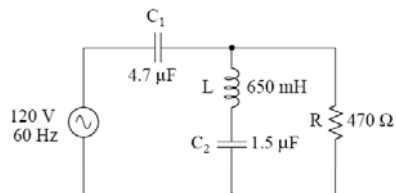

Reactances and Resistances:

$X_{C1} = \frac{1}{2\pi f C_1}$	$X_L = 2\pi f L$
$X_{C1} = \frac{1}{(2)(\pi)(60 \text{ Hz})(4.7 \mu\text{F})}$	$X_L = (2)(\pi)(60 \text{ Hz})(650 \text{ mH})$
$X_{C1} = 564.38 \Omega$	$X_L = 245.04 \Omega$
$X_{C2} = \frac{1}{2\pi f C_2}$	
$X_{C2} = \frac{1}{(2)(\pi)(60 \text{ Hz})(1.5 \mu\text{F})}$	$R = 470 \Omega$
$X_{C2} = 1.7684 \text{ k}\Omega$	

$$Z_{C1} = 0 - j564.38 \Omega \text{ or } 564.38 \Omega \angle -90^\circ$$

$$Z_L = 0 + j245.04 \Omega \text{ or } 245.04 \Omega \angle 90^\circ$$


$$Z_{C2} = 0 - j1.7684 \text{ k}\Omega \text{ or } 1.7684 \text{ k}\Omega \angle -90^\circ$$

$$Z_R = 470 + j0 \Omega \text{ or } 470 \Omega \angle 0^\circ$$

Dr. Levent ÇETİN

L02 Alternating Voltage and Current

AC circuit –Complex Circuit

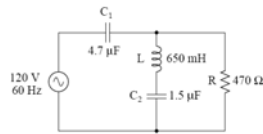

	C ₁	L	C ₂	R	Total	
E					120 + j0 120 ∠ 0°	Volts
I						Amps
Z	0 - j564.38 564.38 ∠ -90°	0 + j245.04 245.04 ∠ 90°	0 - j1.7684k 1.7684k ∠ -90°	470 + j0 470 ∠ 0°		Ohms

The calculation of impedance in this circuit should be completed step by step.

First, serial connection branch of C₂ and L,

afterwards the parallel branch of resistor and last the serial capacitor effects should be calculated.


	L -- C ₂	R // (L -- C ₂)	Total C ₁ -- [R // (L -- C ₂)]	
E			120 + j0 120 ∠ 0°	Volts
I				Amps
Z	0 - j1.5233k 1.5233k ∠ -90°	429.15 - j132.41 449.11 ∠ -17.147°	429.15 - j696.79 818.34 ∠ -58.371°	Ohms

Rule of series circuits: $Z_{L-C_2} = Z_L + Z_{C_2}$
 Rule of parallel circuits: $Z_{R/(L-C_2)} = \frac{1}{\frac{1}{Z_R} + \frac{1}{Z_{L-C_2}}}$
 Rule of series circuits: $Z_{total} = Z_{C_1} + Z_{R/(L-C_2)}$

Dr. Levent ÇETİN

L02 Alternating Voltage and Current

AC circuit –Complex Circuit

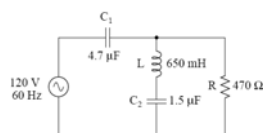

Calculate current drawn from source and passing through C₁

	L -- C ₂	R // (L -- C ₂)	Total C ₁ -- [R // (L -- C ₂)]	
E			120 + j0 120 ∠ 0°	Volts
I			76.899m + j124.86m 146.64m ∠ 58.371°	Amps
Z	0 - j1.5233k 1.5233k ∠ -90°	429.15 - j132.41 449.11 ∠ -17.147°	429.15 - j696.79 818.34 ∠ -58.371°	Ohms

$$\begin{aligned} &\uparrow \\ &\text{Ohm's} \\ &\text{Law} \\ &I = \frac{E}{Z} \end{aligned}$$

Same current is passing through L-C₂ branch


	L -- C ₂	R // (L -- C ₂)	Total C ₁ -- [R // (L -- C ₂)]	
E			120 + j0 120 ∠ 0°	Volts
I		76.899m + j124.86m 146.64m ∠ 58.371°	76.899m + j124.86m 146.64m ∠ 58.371°	Amps
Z	0 - j1.5233k 1.5233k ∠ -90°	429.15 - j132.41 449.11 ∠ -17.147°	429.15 - j696.79 818.34 ∠ -58.371°	Ohms

Rule of series circuits: $I_{total} = I_{C_1} = I_{R/(L-C_2)}$

Dr. Levent ÇETİN

L02 Alternating Voltage and Current

AC circuit –Complex Circuit

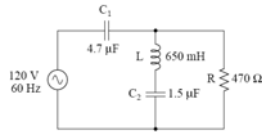Voltage drop on L-C₂ branch

	L -- C ₂	R // (L -- C ₂)	C ₁ -- [R // (L -- C ₂)]	Total	
E		49.533 + j43.400 65.857 ∠ 41.225°	120 + j0 120 ∠ 0°		Volts
I		76.899m + j124.86m 146.64m ∠ 58.371°	76.899m + j124.86m 146.64m ∠ 58.371°		Amps
Z	0 - j1.5233k 1.5233k ∠ -90°	429.15 - j132.41 449.11 ∠ -17.147°	429.15 - j696.79 818.34 ∠ -58.371°		Ohms

Ohm's Law
E = IZ

Same Voltage drops on parallel R branch


	L -- C ₂	R // (L -- C ₂)	C ₁ -- [R // (L -- C ₂)]	Total	
E	49.533 + j43.400 65.857 ∠ 41.225°	49.533 + j43.400 65.857 ∠ 41.225°	120 + j0 120 ∠ 0°		Volts
I		76.899m + j124.86m 146.64m ∠ 58.371°	76.899m + j124.86m 146.64m ∠ 58.371°		Amps
Z	0 - j1.5233k 1.5233k ∠ -90°	429.15 - j132.41 449.11 ∠ -17.147°	429.15 - j696.79 818.34 ∠ -58.371°		Ohms

Rule of parallel circuits:
 $E_{R/(L-C_2)} = E_R = E_{L-C_2}$

Dr. Levent ÇETİN

L02 Alternating Voltage and Current

AC circuit –Complex Circuit

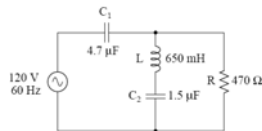

	L -- C ₂	R // (L -- C ₂)	C ₁ -- [R // (L -- C ₂)]	Total	
E	49.533 + j43.400 65.857 ∠ 41.225°	49.533 + j43.400 65.857 ∠ 41.225°	120 + j0 120 ∠ 0°		Volts
I	-28.490m + j32.516m 43.232m ∠ 131.22°	76.899m + j124.86m 146.64m ∠ 58.371°	76.899m + j124.86m 146.64m ∠ 58.371°		Amps
Z	0 - j1.5233k 1.5233k ∠ -90°	429.15 - j132.41 449.11 ∠ -17.147°	429.15 - j696.79 818.34 ∠ -58.371°		Ohms

Ohm's Law
 $I = \frac{E}{Z}$

	C ₁	L	C ₂	R	Total
E					120 + j0 120 ∠ 0°
I					
Z	0 - j1.5233k 1.5233k ∠ -90°	0 + j242.04 242.04 ∠ 90°	0 - j3.768k 3.768k ∠ -90°	470 + j0 470 ∠ 0°	

	C ₁	L	C ₂	R	
E	70.107 + j13.100 82.760 ∠ -31.639°	7.898 + j0.951 10.594 ∠ 7.712°	57.501 + j50.382 76.481 ∠ 41.225°	10.233 + j13.100 65.857 ∠ 41.225°	Volts
I	76.899m + j124.86m 146.64m ∠ 58.371°	-28.490m + j32.516m 43.232m ∠ 131.22°	-28.490m + j32.516m 43.232m ∠ 131.22°	105.39m + j92.341m 140.12m ∠ 41.225°	Amps
Z	0 + j242.04 242.04 ∠ 90°	0 + j242.04 242.04 ∠ 90°	0 + j3.768k 3.768k ∠ 90°	470 + j0 470 ∠ 0°	Ohms

Ohm's Law
E = IZ

Ohm's Law
E = IZ

Dr. Levent ÇETİN

L02 Alternating Voltage and Current

Power in AC circuit


Since it was mentioned, there is a phase shift between current and voltage in AC circuits. The reason is the complex number impedance as it was stated.

So there are three definitions in AC circuits which are related with power.

These are:

- True power (active power),
- Reactive power,
- Apparent power.

Impedance Calculations:

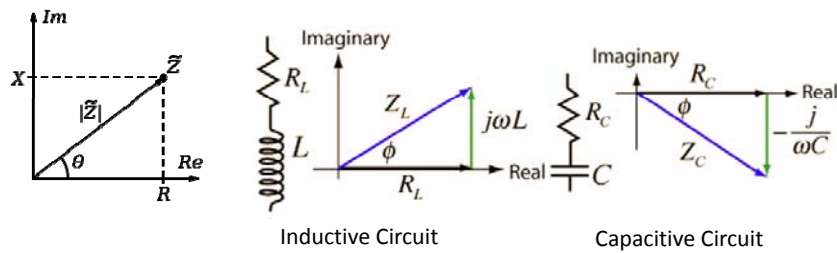

Dr. Levent ÇETİN

L02 Alternating Voltage and Current

Power in AC circuit

$$P = \text{true power} \quad P = I^2 R \quad P = \frac{E^2}{R}$$


Measured in units of Watts

$$Q = \text{reactive power} \quad Q = I^2 X \quad Q = \frac{E^2}{X}$$

Measured in units of Volt-Amps-Reactive (VAR)

$$S = \text{apparent power} \quad S = I^2 Z \quad S = \frac{E^2}{Z} \quad S = IE$$


Measured in units of Volt-Amps (VA)

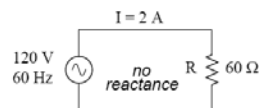

$$P = \text{true power} = I^2 R = 240 \text{ W}$$

$$Q = \text{reactive power} = I^2 X = 0 \text{ VAR}$$
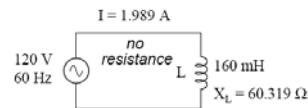
$$S = \text{apparent power} = I^2 Z = 240 \text{ VA}$$



$$P = \text{true power} = I^2 R = 0 \text{ W}$$

$$Q = \text{reactive power} = I^2 X = 238.73 \text{ VAR}$$

$$S = \text{apparent power} = I^2 Z = 238.73 \text{ VA}$$

Dr. Levent ÇETİN

L02 Alternating Voltage and Current

Power in AC circuit

$$P = \text{true power} \quad P = I^2 R \quad P = \frac{E^2}{R}$$

Measured in units of **Watts**


$$Q = \text{reactive power} \quad Q = I^2 X \quad Q = \frac{E^2}{X}$$

Measured in units of **Volt-Amps-Reactive (VAR)**

$$S = \text{apparent power} \quad S = I^2 Z \quad S = \frac{E^2}{Z} \quad S = IE$$

Measured in units of **Volt-Amps (VA)**

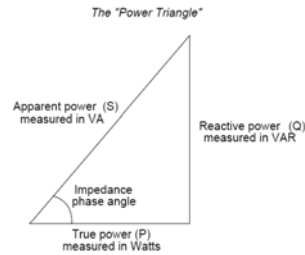The power quantities are scalar quantities. if we consider the 90 degrees of direction angle between the resistor and the reactance and phase shift in the circuit. **This perpendicular triangle is called as 'Power Triangle'**



A part of the power cannot be converted to electrical work in an AC circuit.

The generated effective power is just as the true power.

Power factor is the cosine of the angle between the true and apparent powers ($\cos \phi$).

This value is equal to 1 in only circuits those have just resistors. But if there is a reactance, then the value is between 0 and 1.

Dr. Levent ÇETİN

L02 Alternating Voltage and Current

Power in AC circuit

$$P = \text{true power} \quad P = I^2 R \quad P = \frac{E^2}{R}$$


Measured in units of **Watts**

$$Q = \text{reactive power} \quad Q = I^2 X \quad Q = \frac{E^2}{X}$$

Measured in units of **Volt-Amps-Reactive (VAR)**

$$S = \text{apparent power} \quad S = I^2 Z \quad S = \frac{E^2}{Z} \quad S = IE$$

Measured in units of **Volt-Amps (VA)**

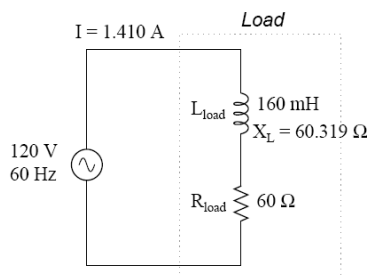

$$P = \text{true power} = I^2 R = 119.365 \text{ W}$$

$$Q = \text{reactive power} = I^2 X = 119.998 \text{ VAR}$$

$$S = \text{apparent power} = I^2 Z = 169.256 \text{ VA}$$

$$\text{Power factor} = \frac{\text{True power}}{\text{Apparent power}}$$

$$\text{Power factor} = \frac{119.365 \text{ W}}{169.256 \text{ VA}}$$

$$\text{Power factor} = 0.705$$


The power factor value shows that the **70.5 % of the power used from the grid is served for the purpose.**

Dr. Levent ÇETİN

L02 Alternating Voltage and Current

Compensation in AC circuit

$P = \text{true power}$ $P = I^2 R$ $P = \frac{E^2}{R}$ <i>Measured in units of Watts</i>	$Q = \text{reactive power}$ $Q = I^2 X$ $Q = \frac{E^2}{X}$ <i>Measured in units of Volt-Amps-Reactive (VAR)</i>	$S = \text{apparent power}$ $S = I^2 Z$ $S = \frac{E^2}{Z}$ $S = IE$ <i>Measured in units of Volt-Amps (VA)</i>
--	---	--

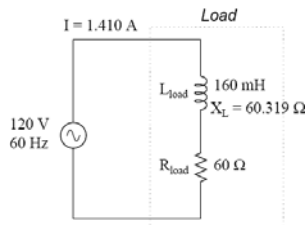

$$P = \text{true power} = I^2 R = 119.365 \text{ W}$$

$$Q = \text{reactive power} = I^2 X = 119.998 \text{ VAR}$$

$$S = \text{apparent power} = I^2 Z = 169.256 \text{ VA}$$

$$\text{Power factor} = \frac{\text{True power}}{\text{Apparent power}}$$

$$\text{Power factor} = \frac{119.365 \text{ W}}{169.256 \text{ VA}}$$

$$\text{Power factor} = 0.705$$

The power factor value shows that the **70.5 % of the power used from the grid is served for the purpose.**

This situation is not wanted.

So, in circuit design stage, it must be noted that the power factor is approximately equal to 1.

For this reason, the capacitive and inductive reactance values should be approximately equal to each other.


If this is not possible, a capacitor or an inductor should be externally added to the circuit. **This improvement is called as compensation.**

Dr. Levent ÇETİN

L02 Alternating Voltage and Current

Compensation in AC circuit

$P = \text{true power}$ $P = I^2 R$ $P = \frac{E^2}{R}$ <i>Measured in units of Watts</i>	$Q = \text{reactive power}$ $Q = I^2 X$ $Q = \frac{E^2}{X}$ <i>Measured in units of Volt-Amps-Reactive (VAR)</i>	$S = \text{apparent power}$ $S = I^2 Z$ $S = \frac{E^2}{Z}$ $S = IE$ <i>Measured in units of Volt-Amps (VA)</i>
--	---	--

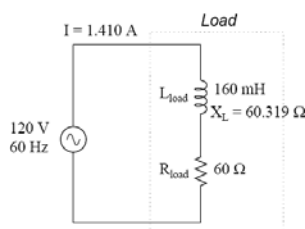

$$P = \text{true power} = I^2 R = 119.365 \text{ W}$$

$$Q = \text{reactive power} = I^2 X = 119.998 \text{ VAR}$$

$$S = \text{apparent power} = I^2 Z = 169.256 \text{ VA}$$

$$\text{Power factor} = \frac{\text{True power}}{\text{Apparent power}}$$

$$\text{Power factor} = \frac{119.365 \text{ W}}{169.256 \text{ VA}}$$

$$\text{Power factor} = 0.705$$

The circuit is inductive so a **parallel** capacitor should be added so that the total reactance of the circuit becomes approximately zero

$$Q = \frac{E^2}{X}$$

... solving for X ...

$$X = \frac{E^2}{Q}$$

$$X = \frac{(120 \text{ V})^2}{119.998 \text{ VAR}}$$

$$X = 120.002 \Omega$$


In parallel branches voltage is constant so the necessary reactance value can be calculated using voltage based power formula

Dr. Levent ÇETİN

L02 Alternating Voltage and Current

Compensation in AC circuit

$P = \text{true power}$ $P = I^2 R$ $P = \frac{E^2}{R}$ <i>Measured in units of Watts</i>	$Q = \text{reactive power}$ $Q = I^2 X$ $Q = \frac{E^2}{X}$ <i>Measured in units of Volt-Amps-Reactive (VAR)</i>	$S = \text{apparent power}$ $S = I^2 Z$ $S = \frac{E^2}{Z}$ $S = IE$ <i>Measured in units of Volt-Amps (VA)</i>
--	---	---

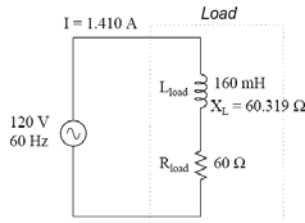

$$P = \text{true power} = I^2 R = 119.365 \text{ W}$$

$$Q = \text{reactive power} = I^2 X = 119.998 \text{ VAR}$$

$$S = \text{apparent power} = I^2 Z = 169.256 \text{ VA}$$

$$\text{Power factor} = \frac{\text{True power}}{\text{Apparent power}}$$

$$\text{Power factor} = \frac{119.365 \text{ W}}{169.256 \text{ VA}}$$

$$\text{Power factor} = 0.705$$

The calculated reactance value is used to find capacitor value

$$X_C = \frac{1}{2\pi f C}$$

... solving for C ...

$$C = \frac{1}{2\pi f X_C}$$

$$C = \frac{1}{2\pi(60 \text{ Hz})(120.002 \Omega)}$$


$$C = 22.105 \mu\text{F}$$

Dr. Levent ÇETİN

L02 Alternating Voltage and Current

Compensation in AC circuit

$P = \text{true power}$ $P = I^2 R$ $P = \frac{E^2}{R}$ <i>Measured in units of Watts</i>	$Q = \text{reactive power}$ $Q = I^2 X$ $Q = \frac{E^2}{X}$ <i>Measured in units of Volt-Amps-Reactive (VAR)</i>	$S = \text{apparent power}$ $S = I^2 Z$ $S = \frac{E^2}{Z}$ $S = IE$ <i>Measured in units of Volt-Amps (VA)</i>
--	---	---

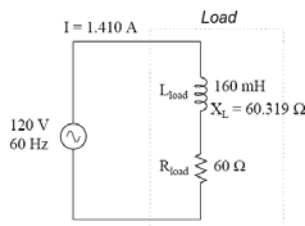

$$P = \text{true power} = I^2 R = 119.365 \text{ W}$$

$$Q = \text{reactive power} = I^2 X = 119.998 \text{ VAR}$$


$$S = \text{apparent power} = I^2 Z = 169.256 \text{ VA}$$

$$\text{Power factor} = \frac{\text{True power}}{\text{Apparent power}}$$

$$\text{Power factor} = \frac{119.365 \text{ W}}{169.256 \text{ VA}}$$

$$\text{Power factor} = 0.705$$

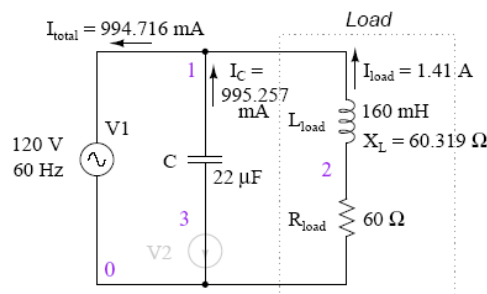
The capacitor value found is not a standard value for capacitors, so the closest standard value should be chosen (22 μF) and connected in parallel with the circuit.



Dr. Levent ÇETİN

L02 Alternating Voltage and Current

Compensation in AC circuit

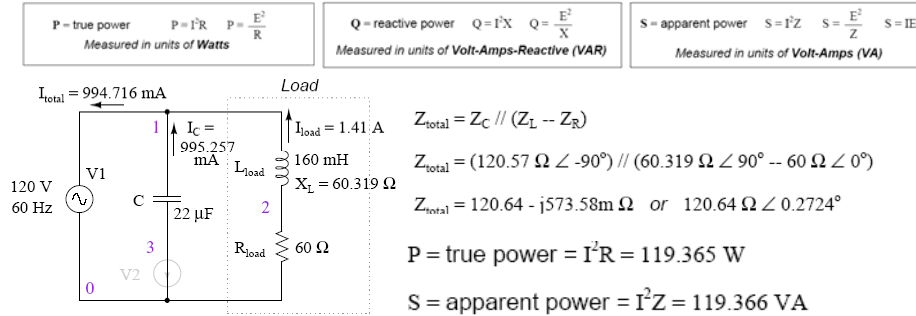

$$\text{Power factor} = \frac{\text{True power}}{\text{Apparent power}}$$

$$\text{Power factor} = \frac{119.365 \text{ W}}{119.366 \text{ VA}}$$


$$\text{Power factor} = 0.9999887$$

this improvement made the power factor closer to 1. Besides, the current is decreased.

Dr. Levent ÇETİN

L02 Alternating Voltage and Current

Compensation in AC circuit

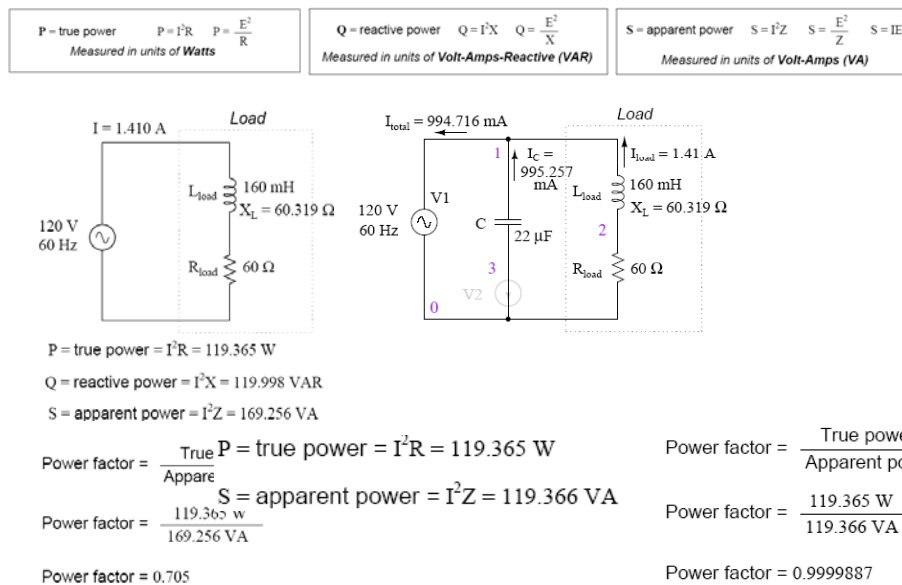

Dr. Levent ÇETİN